

IT5002

Computer Systems and Applications

Datapath Design

colintan@nus.edu.sg




Q & A

- **DO NOT** use the Zoom chat for questions. It doesn't appear in the video recordings.
- Please ask questions at <https://sets.netlify.app/module/61597486a7805d9fb1b4accd>



← OR scan this QR code (may be obscured on some slides)

Lecture #7: Datapath Design

- 1. Building a Processor: Datapath & Control**
- 2. MIPS Processor: Implementation**
- 3. Instruction Execution Cycle (Recap)**
- 4. MIPS Instruction Execution**
- 5. Let's Build a MIPS Processor**
 - 5.1 Fetch Stage
 - 5.2 Decode Stage
 - 5.3 ALU Stage
 - 5.4 Memory Stage
 - 5.5 Register Write Stage
-  **6. The Complete Datapath!**

1. Building a Processor: Datapath & Control

■ Two major components for a processor

Datapath

- Collection of components that process data
- Performs the arithmetic, logical and memory operations

Control

- Tells the datapath, memory and I/O devices what to do according to program instructions




2. MIPS Processor: Implementation

- Simplest possible implementation of a subset of the core MIPS ISA:
 - **Arithmetic and Logical operations**
 - `add, sub, and, or, addi, andi, ori, slt`
 - **Data transfer instructions**
 - `lw, sw`
 - **Branches**
 - `beq, bne`
- Shift instructions (`sll, srl`) and J-type instructions (`j`) will not be discussed:
 - Left as exercises 😊



3. Instruction Execution Cycle (Basic)

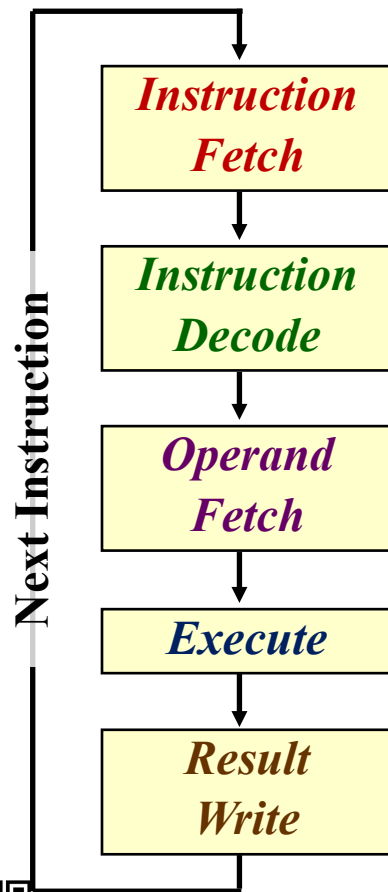

1. **Fetch:**
 - Get instruction from memory
 - Address is in Program Counter (PC) Register
2. **Decode:**
 - Find out the operation required
3. **Operand Fetch:**
 - Get operand(s) needed for operation
4. **Execute:**
 - Perform the required operation
5. **Result Write (Store):**
 - Store the result of the operation

4. MIPS Instruction Execution (1/2)

- Show the actual steps for 3 representative MIPS instructions
- Fetch and Decode stages not shown:
 - The standard steps are performed

	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20(\$1)</code>	<code>beq \$1, \$2, ofst</code>
Fetch	<i>standard</i>	<i>standard</i>	<i>standard</i>
Decode			
Operand Fetch	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> ○ Read [\$1] as <i>opr1</i> ○ Read [\$2] as <i>opr2</i>
Execute	$Result = opr1 + opr2$	<ul style="list-style-type: none"> ○ $MemAddr = opr1 + opr2$ ○ Use <i>MemAddr</i> to read from memory 	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) + ofst \times 4$
Result Write	<i>Result</i> stored in \$3	<i>Memory data</i> stored in \$3	if (<i>Taken</i>) $PC = Target$

opr = operand

MemAddr = Memory Address

■ **ofst** = offset

4. MIPS Instruction Execution (2/2)

- Design changes:
 - Merge *Decode* and *Operand Fetch* – Decode is simple for MIPS
 - Split *Execute* into *ALU* (Calculation) and *Memory Access*

	<code>add \$3, \$1, \$2</code>	<code>lw \$3, 20(\$1)</code>	<code>beq \$1, \$2, ofst</code>
Fetch	Read inst. at [PC]	Read inst. at [PC]	Read inst. at [PC]
Decode & Operand Fetch	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Read [\$2] as <i>opr2</i> 	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Use 20 as <i>opr2</i> 	<ul style="list-style-type: none"> Read [\$1] as <i>opr1</i> Read [\$2] as <i>opr2</i>
ALU	$Result = opr1 + opr2$	$MemAddr = opr1 + opr2$	$Taken = (opr1 == opr2) ?$ $Target = (PC+4) + ofst \times 4$
Memory Access		Use <i>MemAddr</i> to read from memory	
Result Write	<i>Result</i> stored in \$3	<i>Memory data</i> stored in \$3	if (<i>Taken</i>) $PC = Target$

5. Let's Build a MIPS Processor

■ What we are going to do:

- Look at each stage closely, figure out the requirements and processes
- Sketch a high level block diagram, then zoom in for each elements
- With the simple starting design, check whether different type of instructions can be handled:
 - **Add modifications when needed**

→ Study the design from the viewpoint of a designer, instead of a "tourist" 😊



5.1 Fetch Stage: Requirements

1. **Fetch**
2. Decode
3. ALU
4. Memory
5. RegWrite

■ Instruction **Fetch Stage**:

1. Use the **Program Counter (PC)** to fetch the instruction from **memory**

- PC is implemented as a special register in the processor

2. **Increment** the PC by 4 to get the address of the next instruction:


- How do we know the next instruction is at PC+4?
- Note the exception when branch/jump instruction is executed

■ Output to the next stage (**Decode**):

- The instruction to be executed




5.1 Fetch Stage: Block Diagram

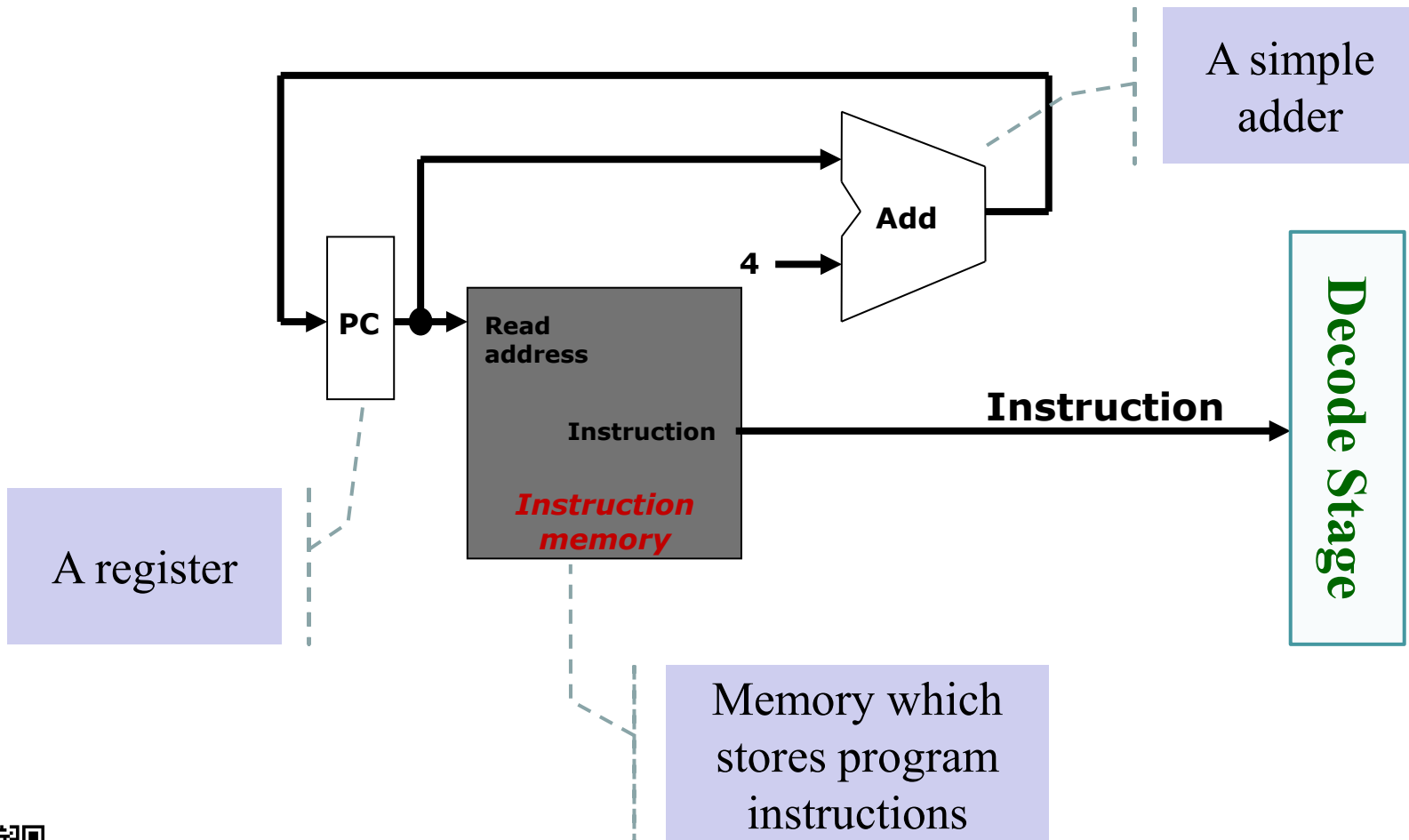

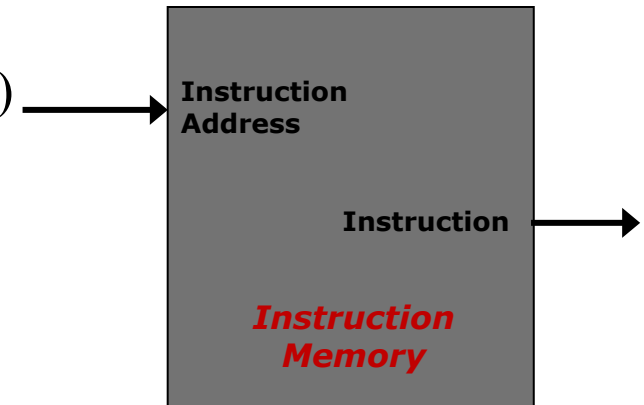5.1 Element: Instruction Memory

- Storage element for the instructions
 - It is a **sequential circuit** (to be covered later)
 - Has an internal state that stores information
 - Clock signal is assumed and not shown



- Supply instruction given the address
 - Given instruction address M as input, the memory outputs the content at address M
 - Conceptual diagram of the memory layout is given on the right →


Memory	

2048	add \$3, \$1, \$2
2052	sll \$4, \$3, 2
2056	andi \$1, \$4, 0xF
.....



 
5.1 Element: Adder

- Combinational logic to implement the addition of two numbers
- **Inputs:**
 - Two 32-bit numbers **A**, **B**
- **Output:**
 - Sum of the input numbers, **A + B**



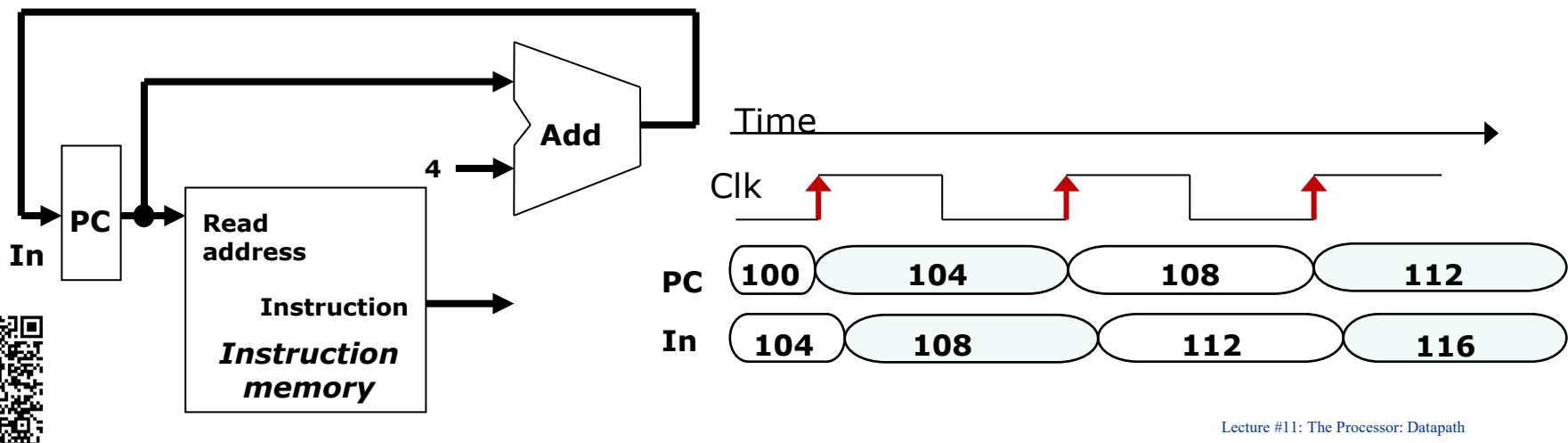5.1 The Idea of Clocking

- It seems that we are reading and updating the PC at the same time:
 - How can it work properly?
- Magic of clock:**
 - PC is read during the first half of the clock period and it is updated with $PC+4$ at the **next rising clock edge**



5.2 Decode Stage: Requirements

- **Instruction Decode Stage:**

- Gather data from the instruction fields:

1. Read the **opcode** to determine instruction type and field lengths
2. Read data from all necessary registers
 - Can be two (e.g. **add**), one (e.g. **addi**) or zero (e.g. **j**)

- **Input from previous stage (Fetch):**

- Instruction to be executed


- **Output to the next stage (ALU):**

- Operation and the necessary operands

1. Fetch
2. **Decode**
3. ALU
4. Memory
5. RegWrite




5.2 Decode Stage: Block Diagram

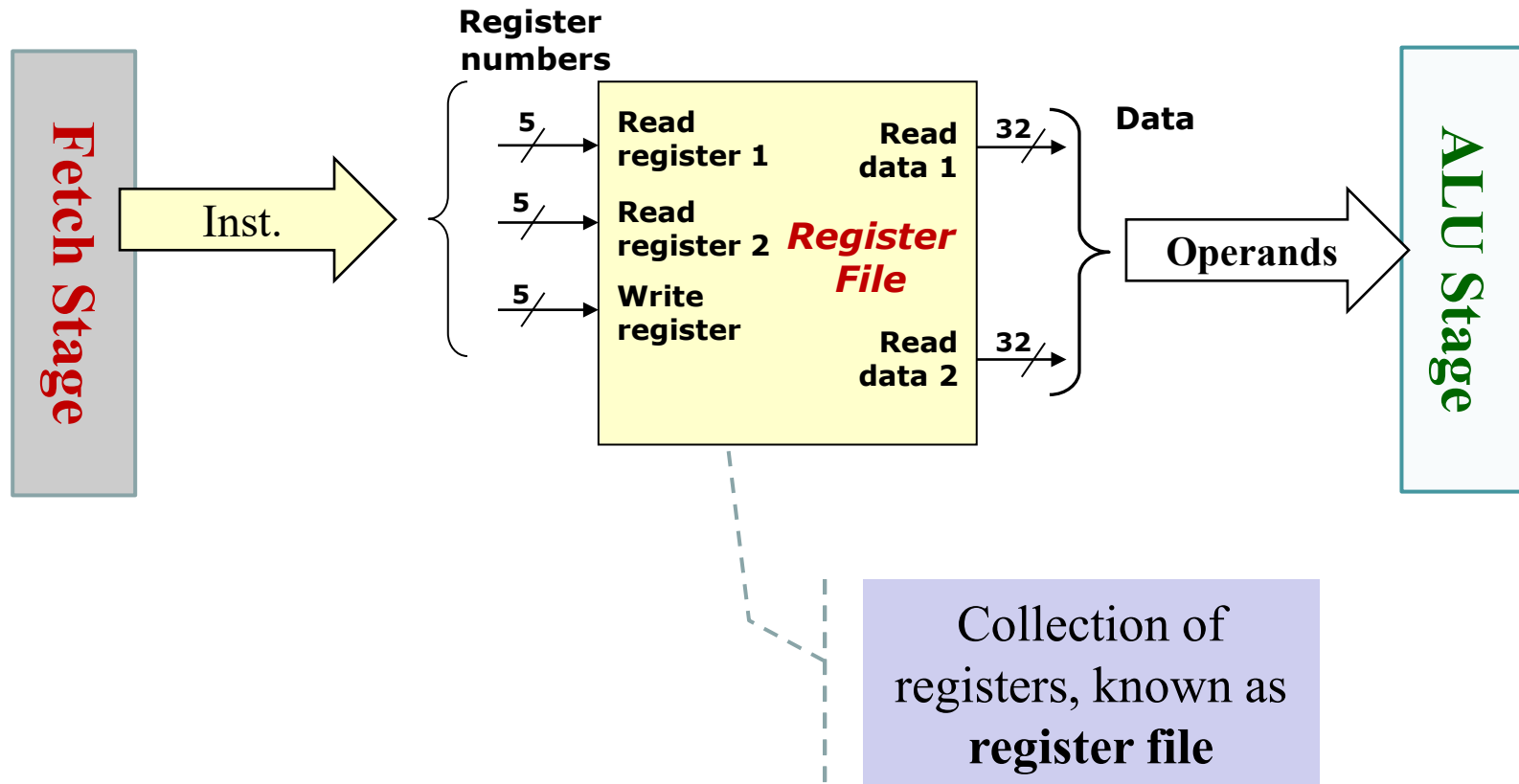


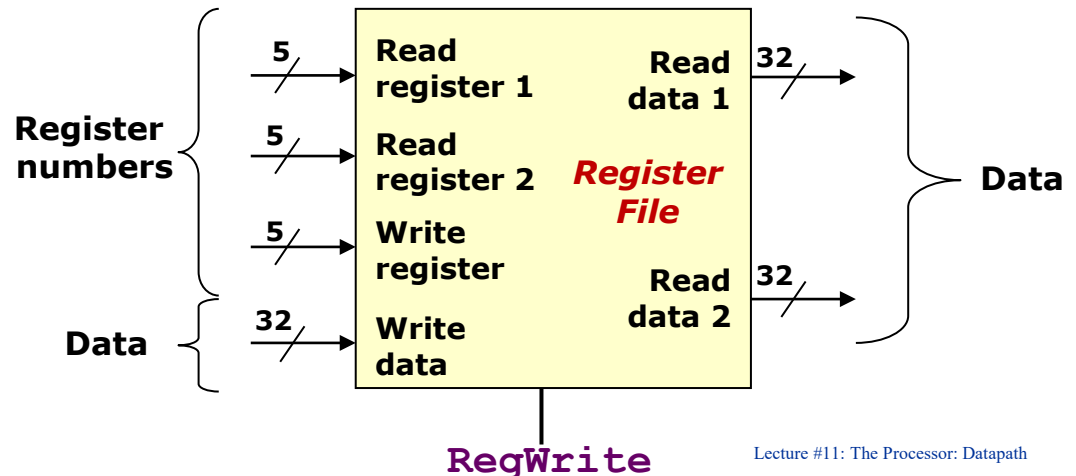5.2 Element: Register File


- A collection of 32 registers:
 - Each 32-bit wide; can be read/written by specifying register number
 - Read at most two registers per instruction
 - Write at most one register per instruction
- **RegWrite** is a control signal to indicate:
 - Writing of register
 - 1(True) = Write, 0 (False) = No Write



5.2 Decode Stage: R-Format Instruction

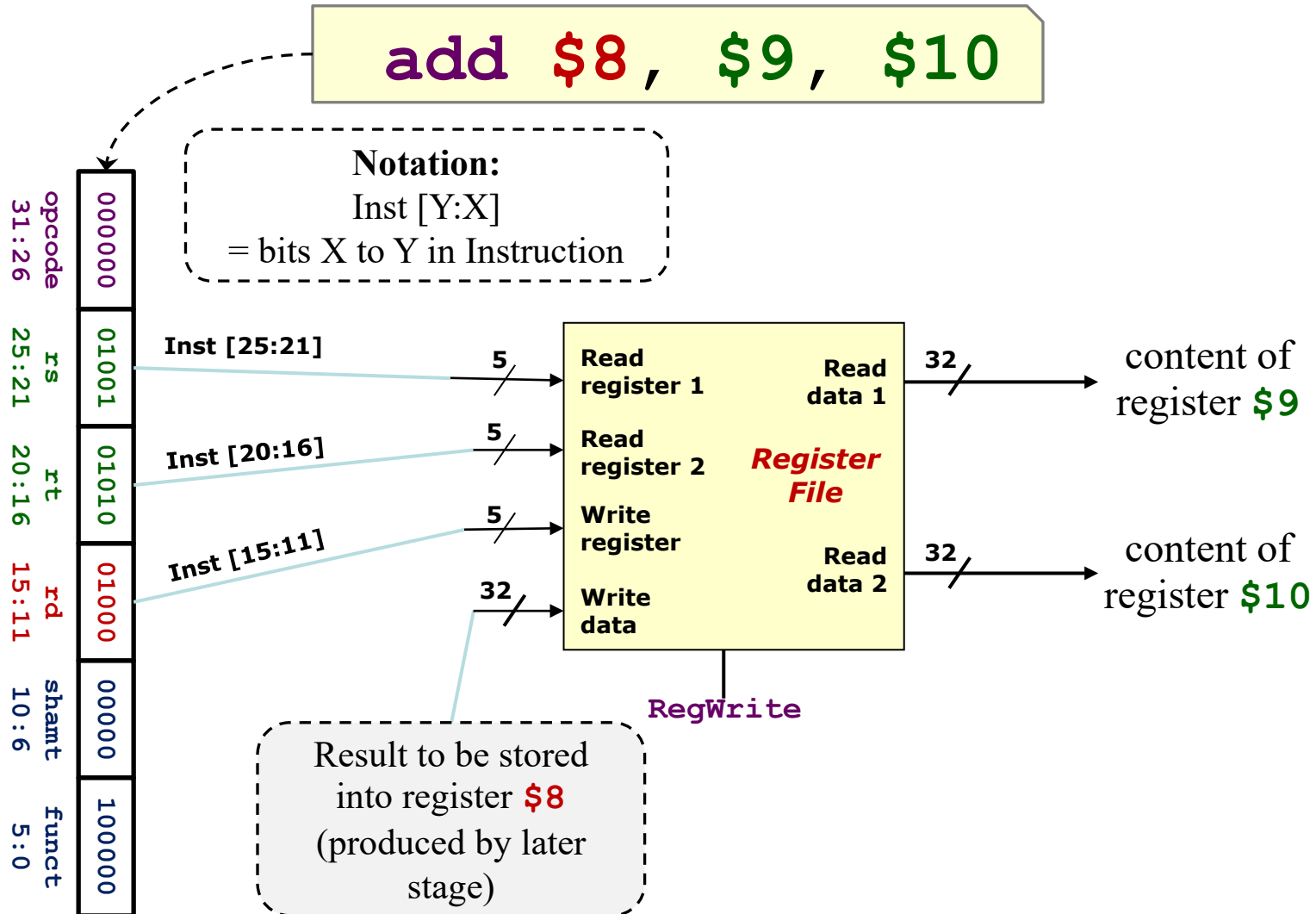

5.2 Decode Stage: I-Format Instruction

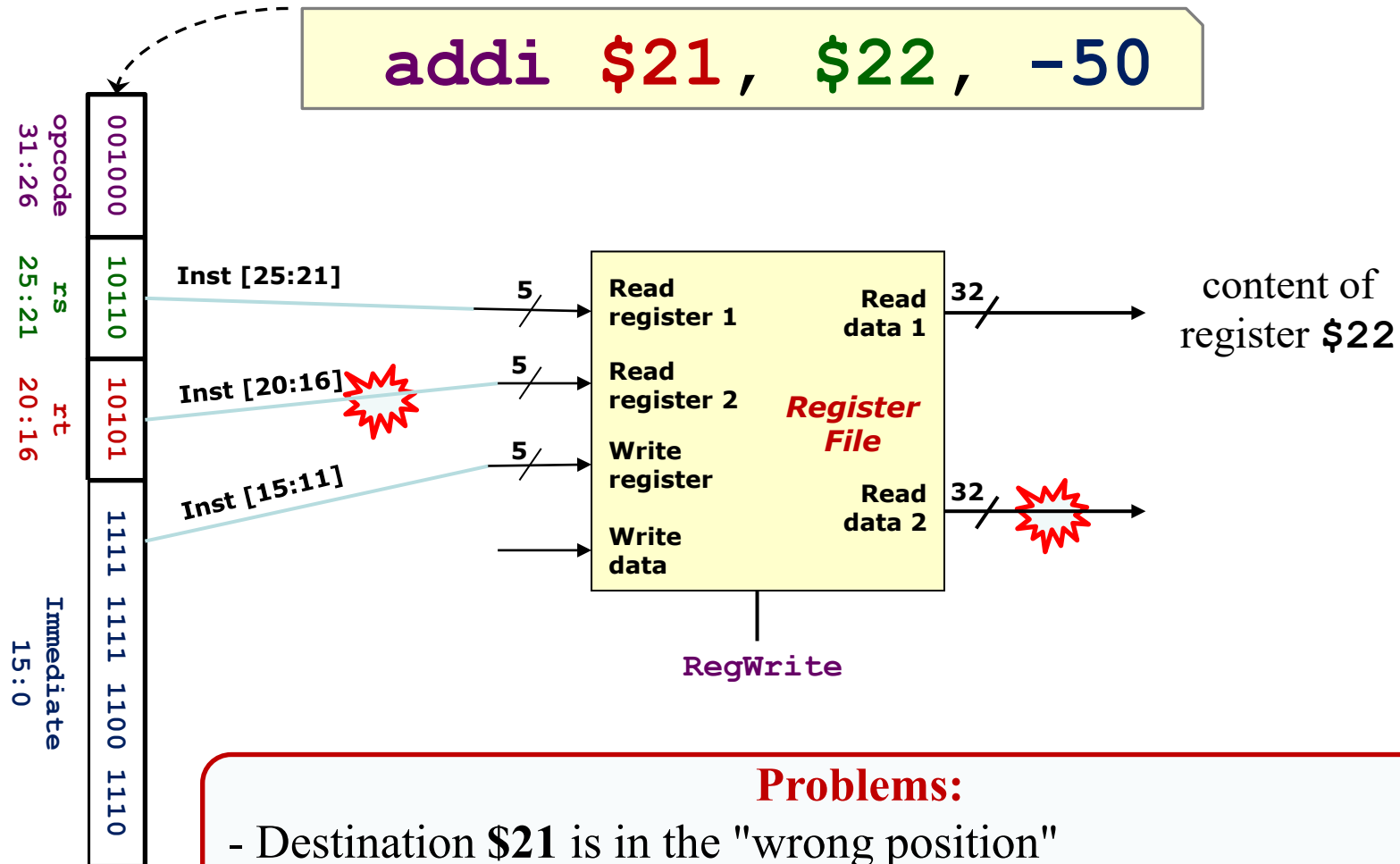


Problems:

- Destination \$21 is in the "wrong position"
- **Read Data 2** is an immediate value, not from register

5.2 Decode Stage: Choice in Destination

addi \$21, \$22, -50

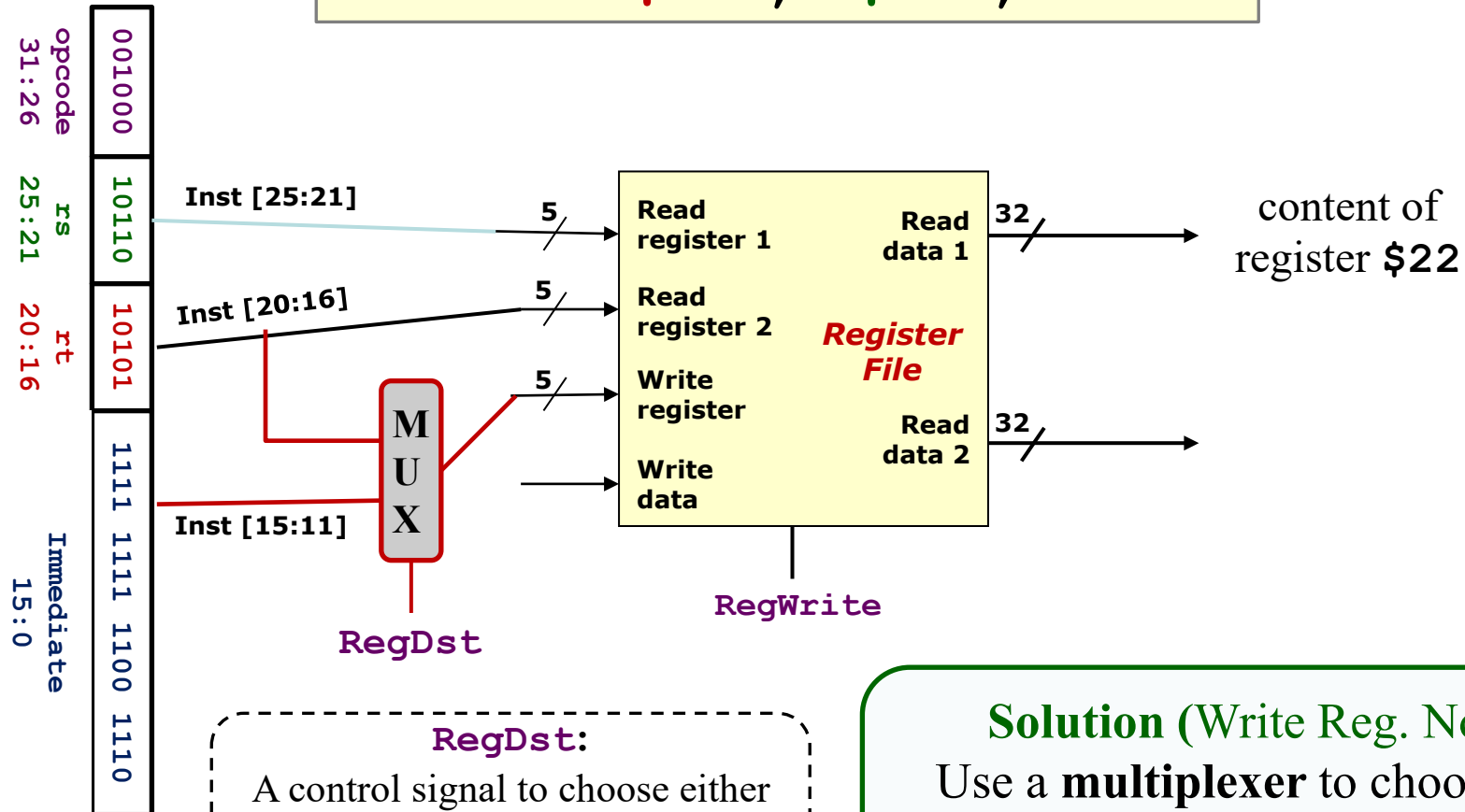

RegDst:

A control signal to choose either **Inst[20:16]** or **Inst[15:11]** as the write register number

Solution (Write Reg. No.):

Use a **multiplexer** to choose the correct write register number based on instruction type



5.2 Multiplexer

- **Function:**

- Selects one input from multiple input lines

- **Inputs:**


- n lines of same width

- **Control:**

- m bits where $n = 2^m$

- **Output:**

 - Select i^{th} input line if control = i




Control=0 \rightarrow select in_0 to out

Control=3 \rightarrow select in_3 to out



5.2 Decode Stage: Choice in Data 2

addi \$21, \$22, -50

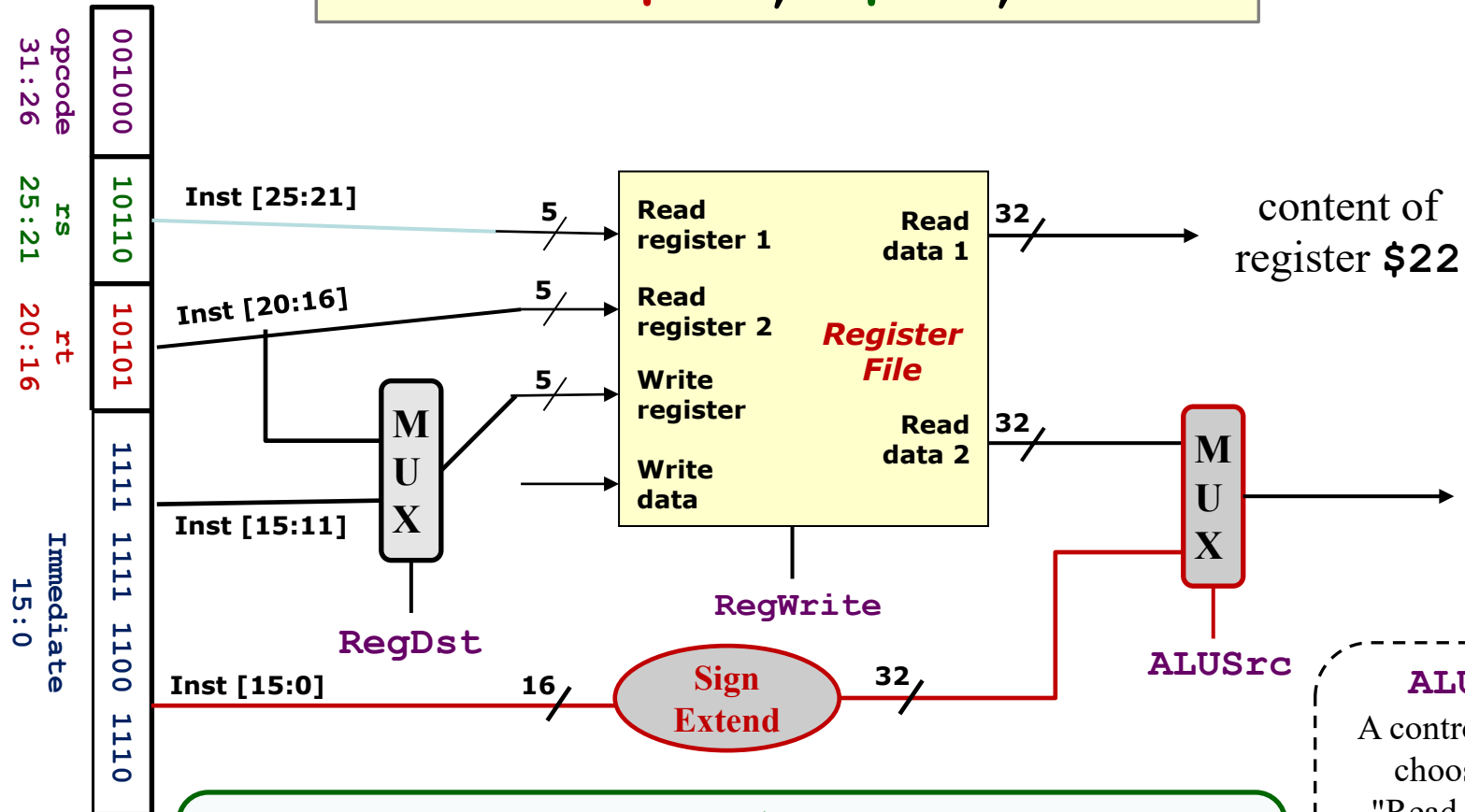

Solution (Rd. Data 2):

Use a **multiplexer** to choose the correct operand 2.
 Sign extend the 16-bit immediate value to 32-bit

ALUSrc:


A control signal to choose either "Read data 2" or the sign extended Inst[15:0] as the second operand



5.2 Decode Stage: Load Word Instruction


lw \$21, -50(\$22)

Do we need any modification?

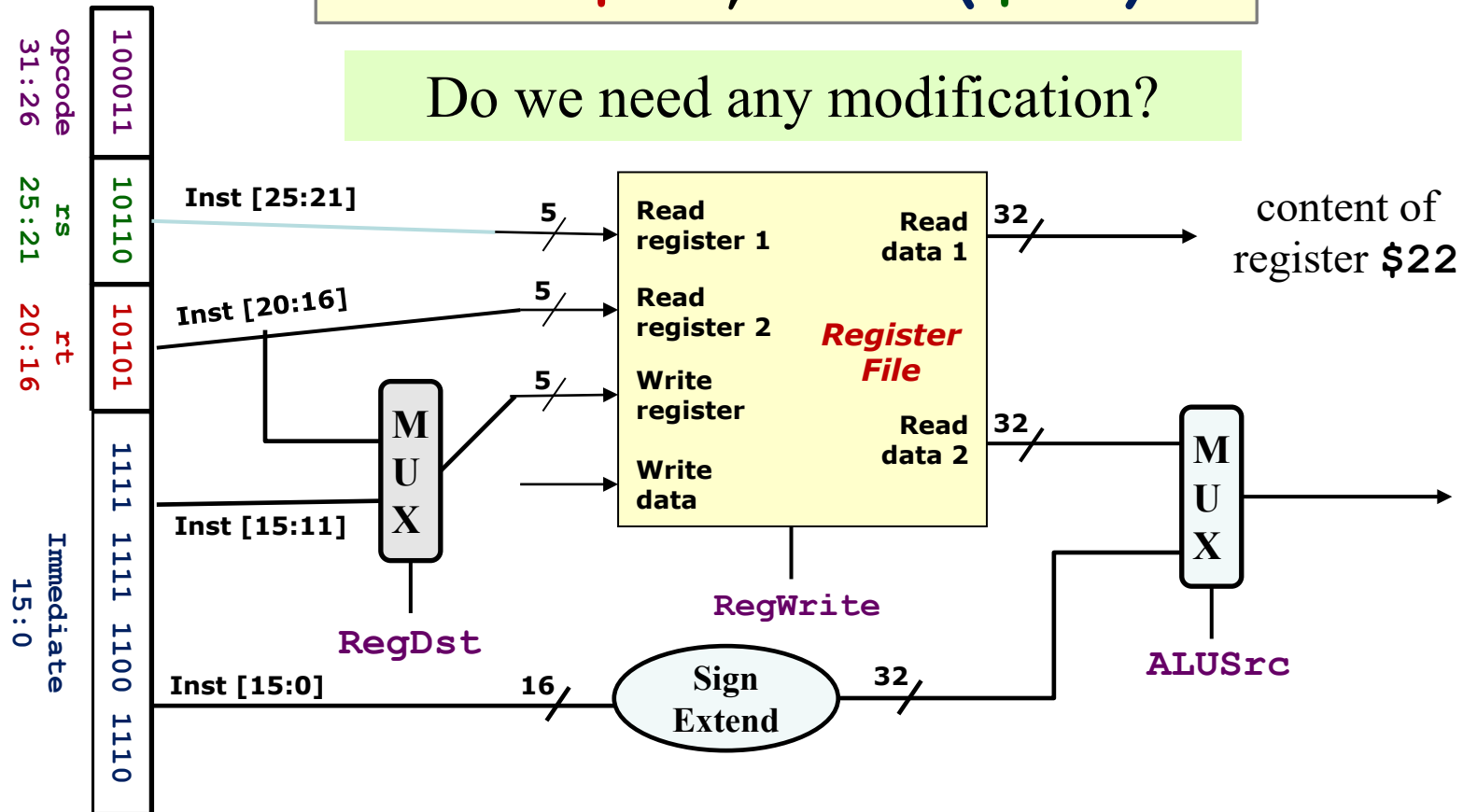

5.2 Decode Stage: Branch Instruction


beq \$9, \$0, 3

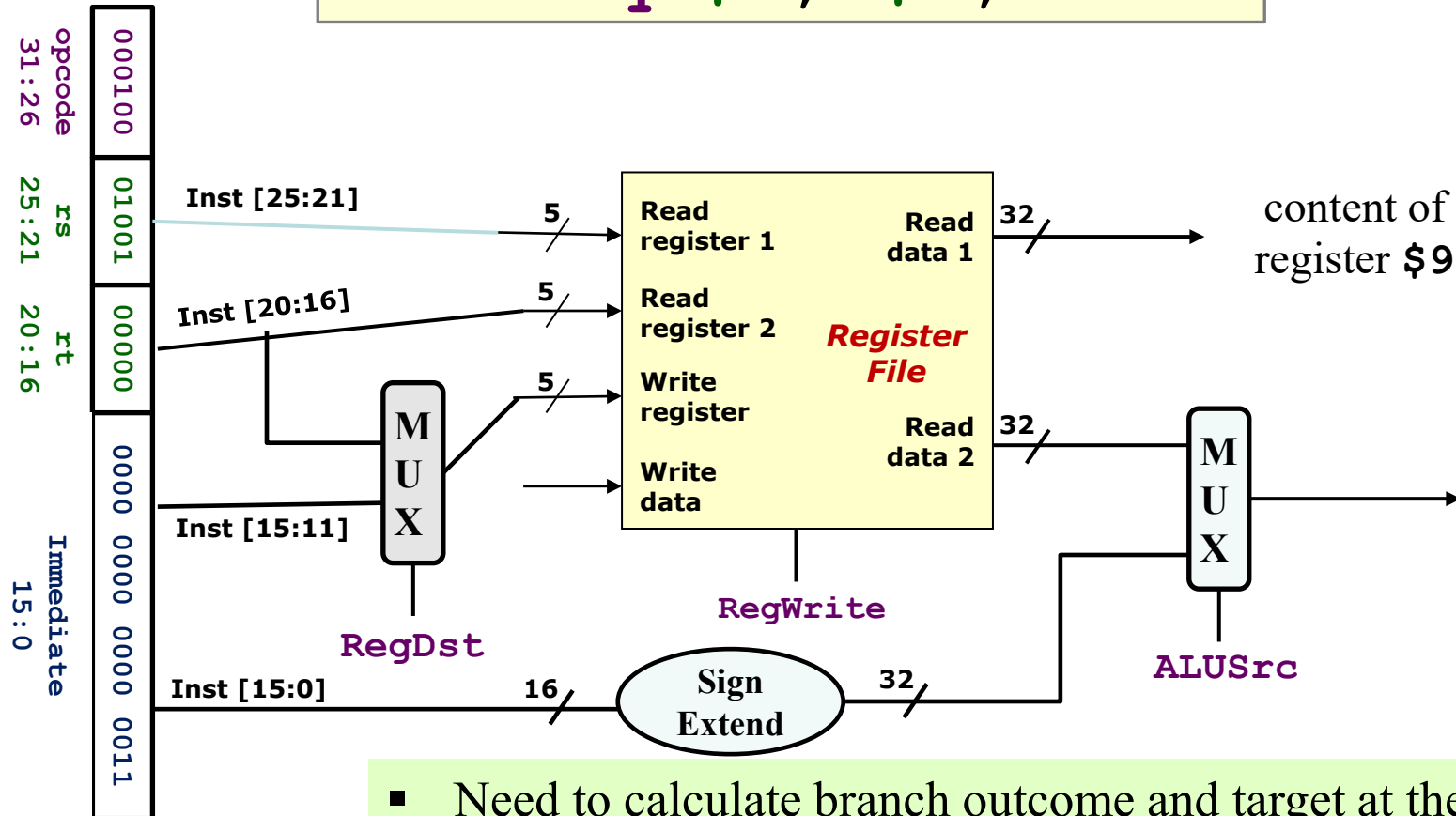

- Need to calculate branch outcome and target at the same time!
- We will tackle this problem at the ALU stage



5.2 Decode Stage: Summary

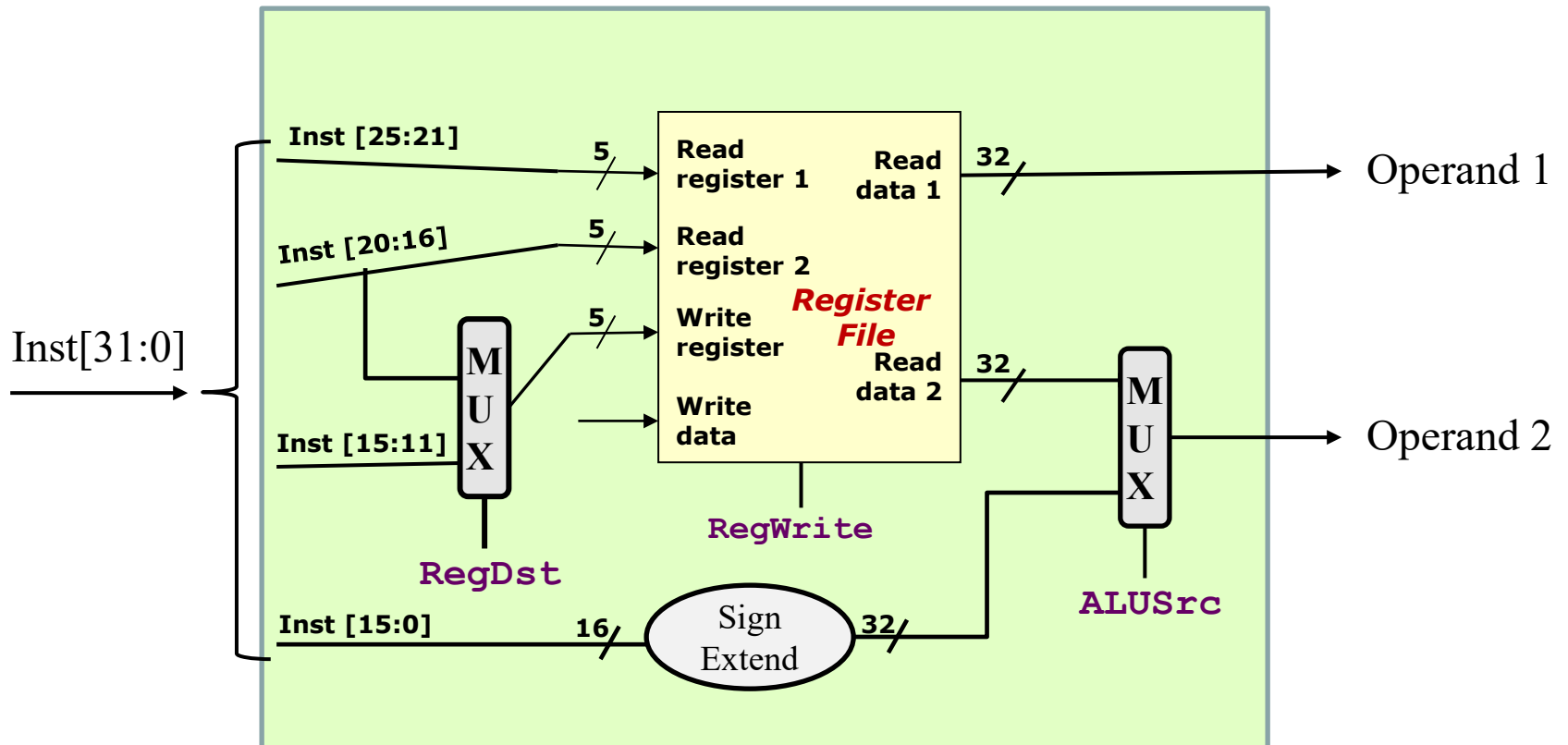

5.3 ALU Stage: Requirements

- **Instruction ALU Stage:**

- ALU = Arithmetic-Logic Unit
- Also called the **Execution stage**
- Perform the real work for most instructions here
 - **Arithmetic (e.g. add, sub), Shifting (e.g. sll), Logical (e.g. and, or)**
 - **Memory operation (e.g. lw, sw): Address calculation**
 - **Branch operation (e.g. bne, beq): Perform register comparison and target address calculation**

- **Input from previous stage (Decode):**

- Operation and Operand(s)


- **Output to the next stage (Memory):**

- Calculation result

1. Fetch
2. Decode
- 3. ALU**
4. Memory
5. RegWrite




5.3 ALU Stage: Block Diagram

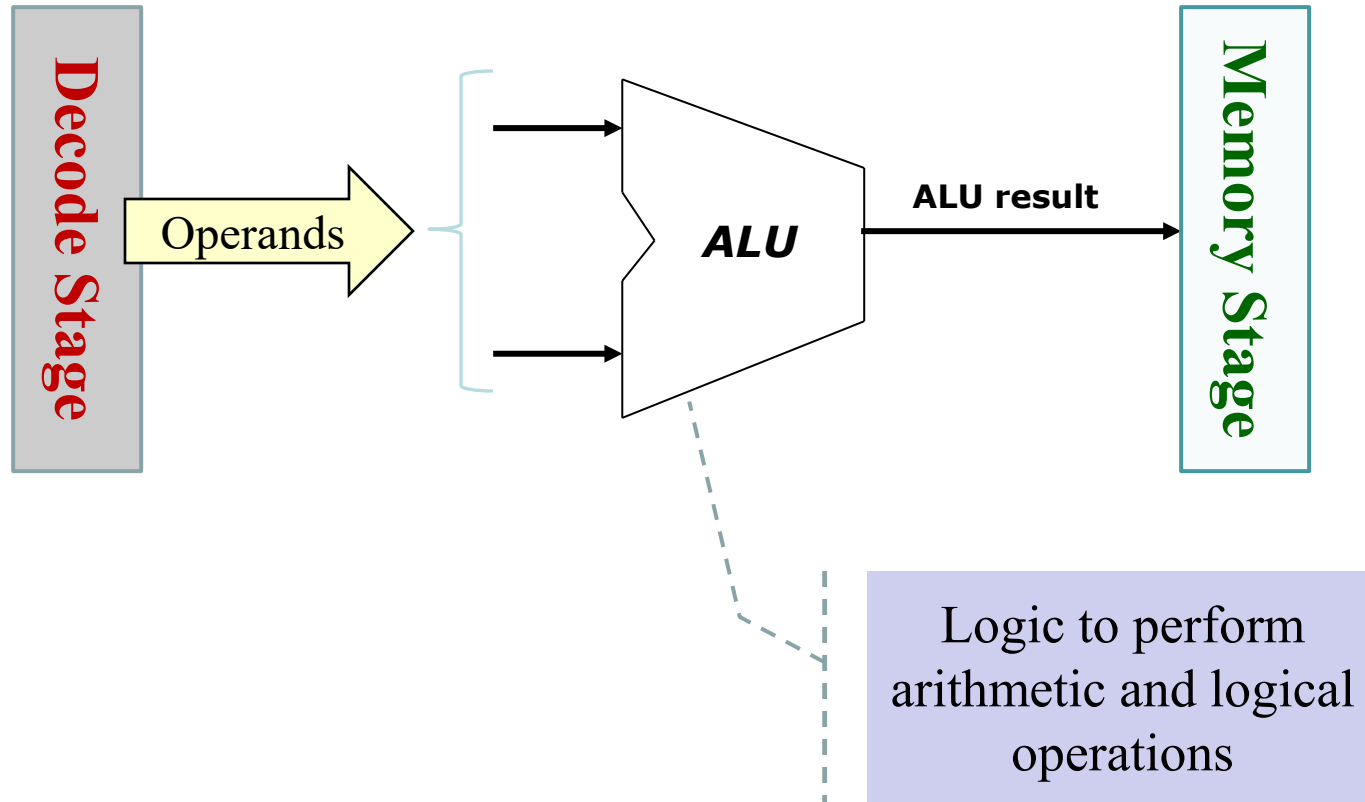

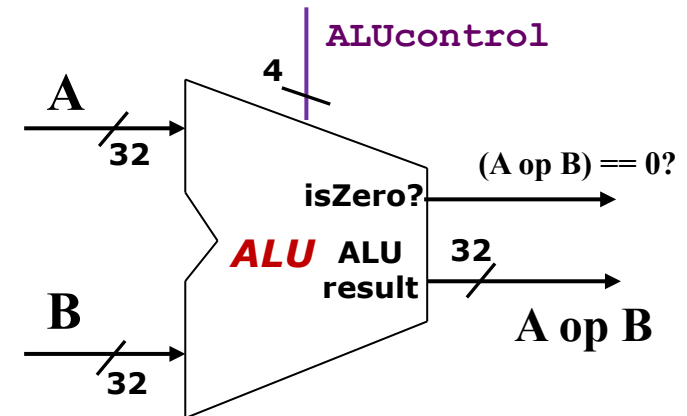5.3 Element: Arithmetic Logic Unit

- **ALU (Arithmetic Logic Unit)**
 - Combinational logic to implement arithmetic and logical operations
- **Inputs:**
 - Two 32-bit numbers
- **Control:**
 - 4-bit to decide the particular operation
- **Outputs:**
 - Result of arithmetic/logical operation
 - A 1-bit signal to indicate whether result is zero




ALUcontrol	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	slt
1100	NOR



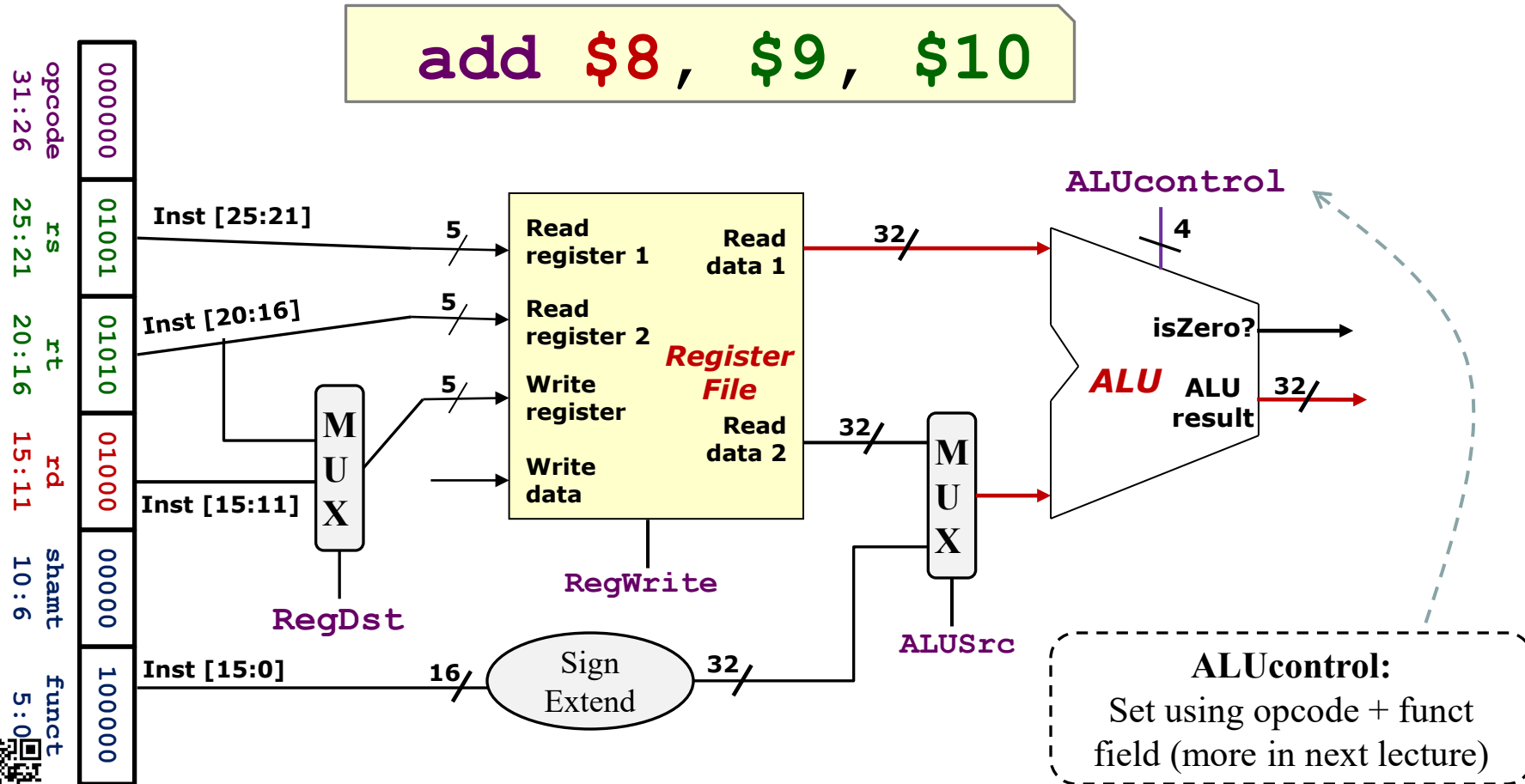5.3 ALU Stage: Non-Branch Instructions

- We can handle non-branch instructions easily:



5.3 ALU Stage: Branch Instructions

- Branch instruction is harder as we need to perform two calculations:
- Example: "**beq** \$9, \$0, 3"

1. Branch Outcome:

- Use ALU to compare the register
- The 1-bit "**isZero?**" signal is enough to handle equal/not equal check (how?)

2. Branch Target Address:


- Introduce additional logic to calculate the address
- Need PC (from **Fetch Stage**)
- Need Offset (from **Decode Stage**)



Complete ALU Stage

115002 Lecture 7 - Datapath Design

Page: 31

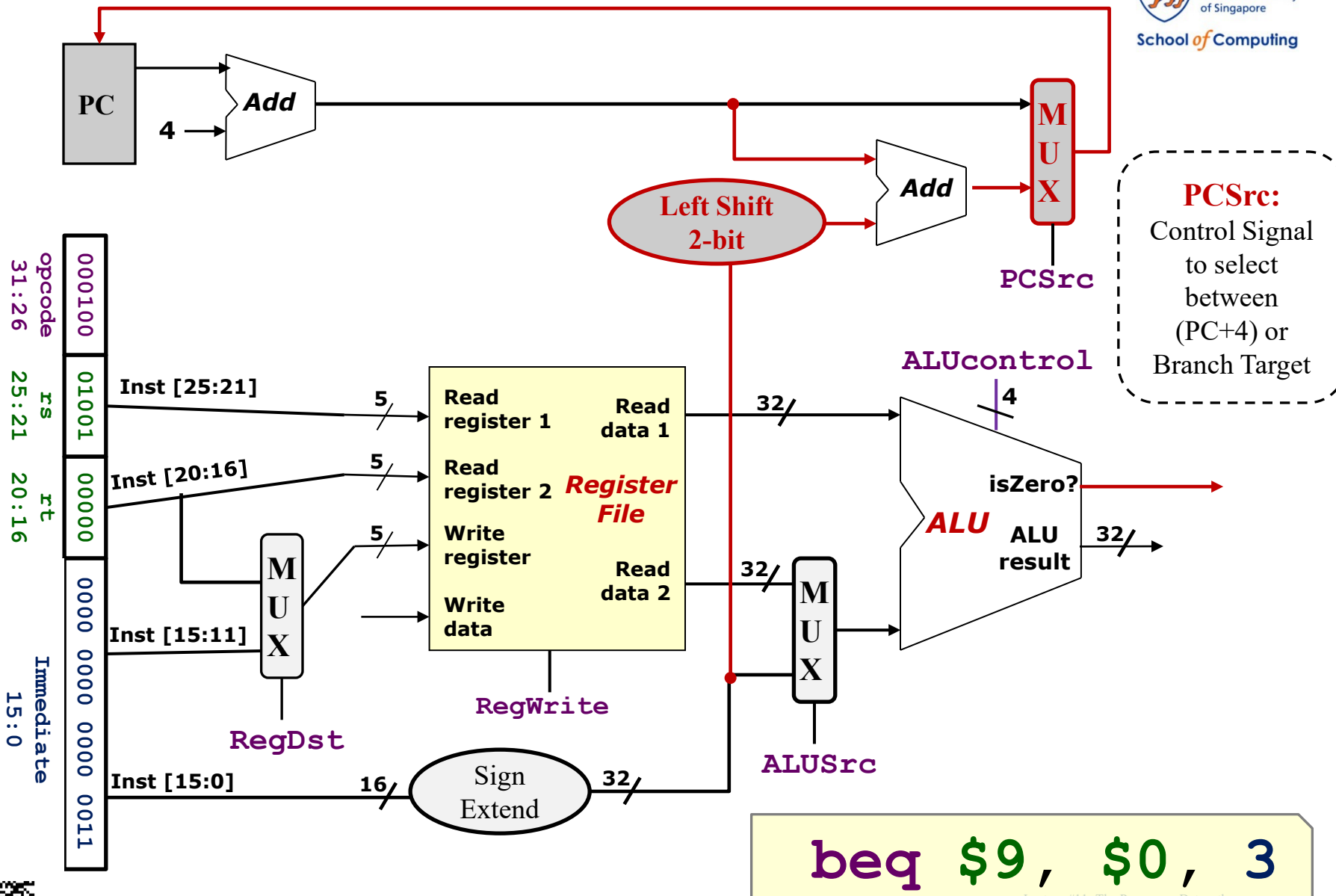


5.4 Memory Stage: Requirements

1. Fetch
2. Decode
3. ALU
- 4. Memory**
5. RegWrite

- **Instruction Memory Access Stage:**
 - Only the **load** and **store** instructions need to perform operation in this stage:
 - Use memory address calculated by ALU Stage
 - Read from or write to data memory
 - All other instructions remain idle
 - Result from ALU Stage will pass through to be used in Register Write stage (see section 5.5) if applicable
- **Input from previous stage (ALU):**
 - Computation result to be used as memory address (if applicable)
- **Output to the next stage (Register Write):**
 - Result to be stored (if applicable)



5.4 Memory Stage: Block Diagram

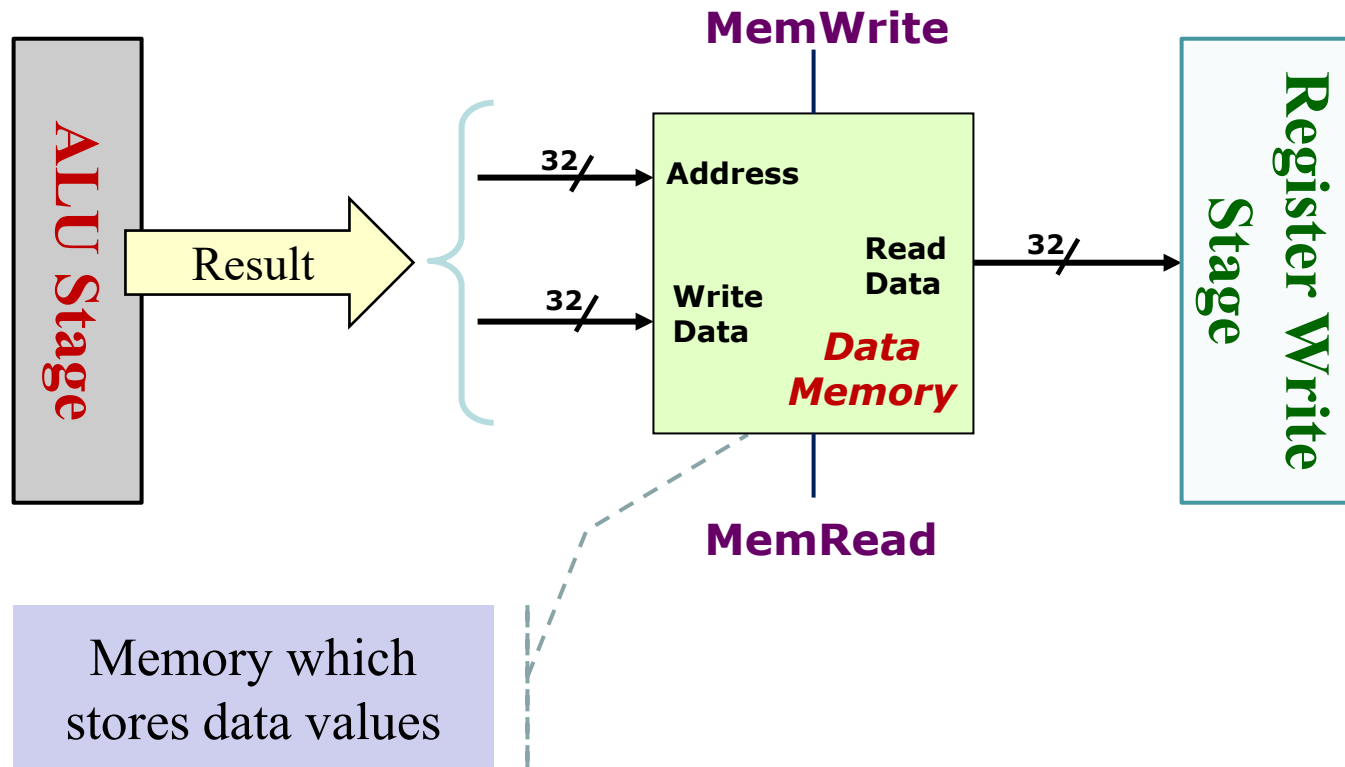

5.4 Element: Data Memory

- Storage element for the data of a program

- Inputs:**


- Memory Address
- Data to be written (Write Data) for store instructions

- Control:**

- Read and Write controls; only one can be asserted at any point of time

- Output:**

 
- Data read from memory (Read Data) for load instructions



5.4 Memory Stage: Load Instruction

- Only relevant parts of Decode and ALU Stages are shown


lw \$21, -50 (\$22)

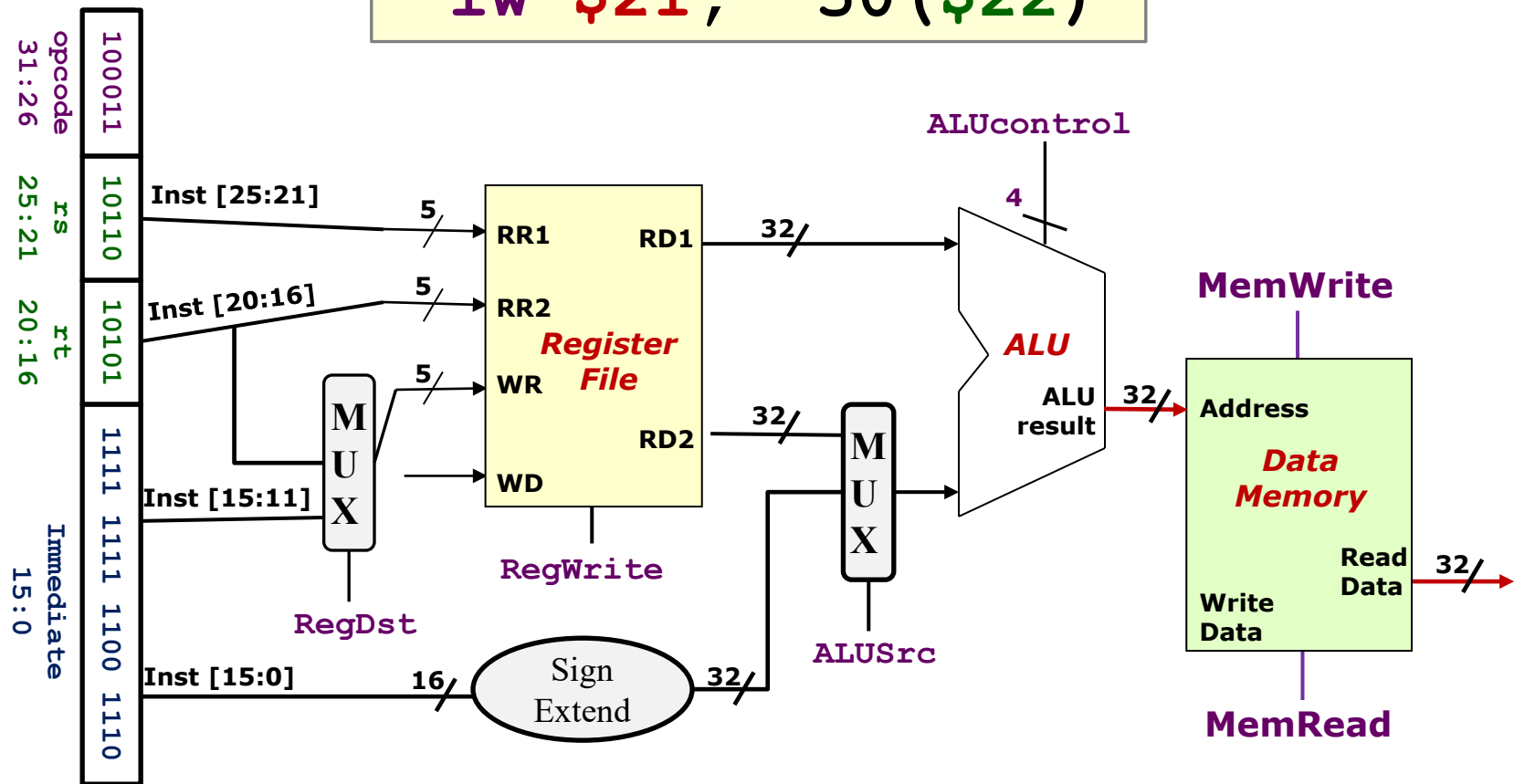

5.4 Memory Stage: Store Instruction

- Need *Read Data 2* (from Decode stage) as the *Write Data*


SW \$21, -50 (\$22)

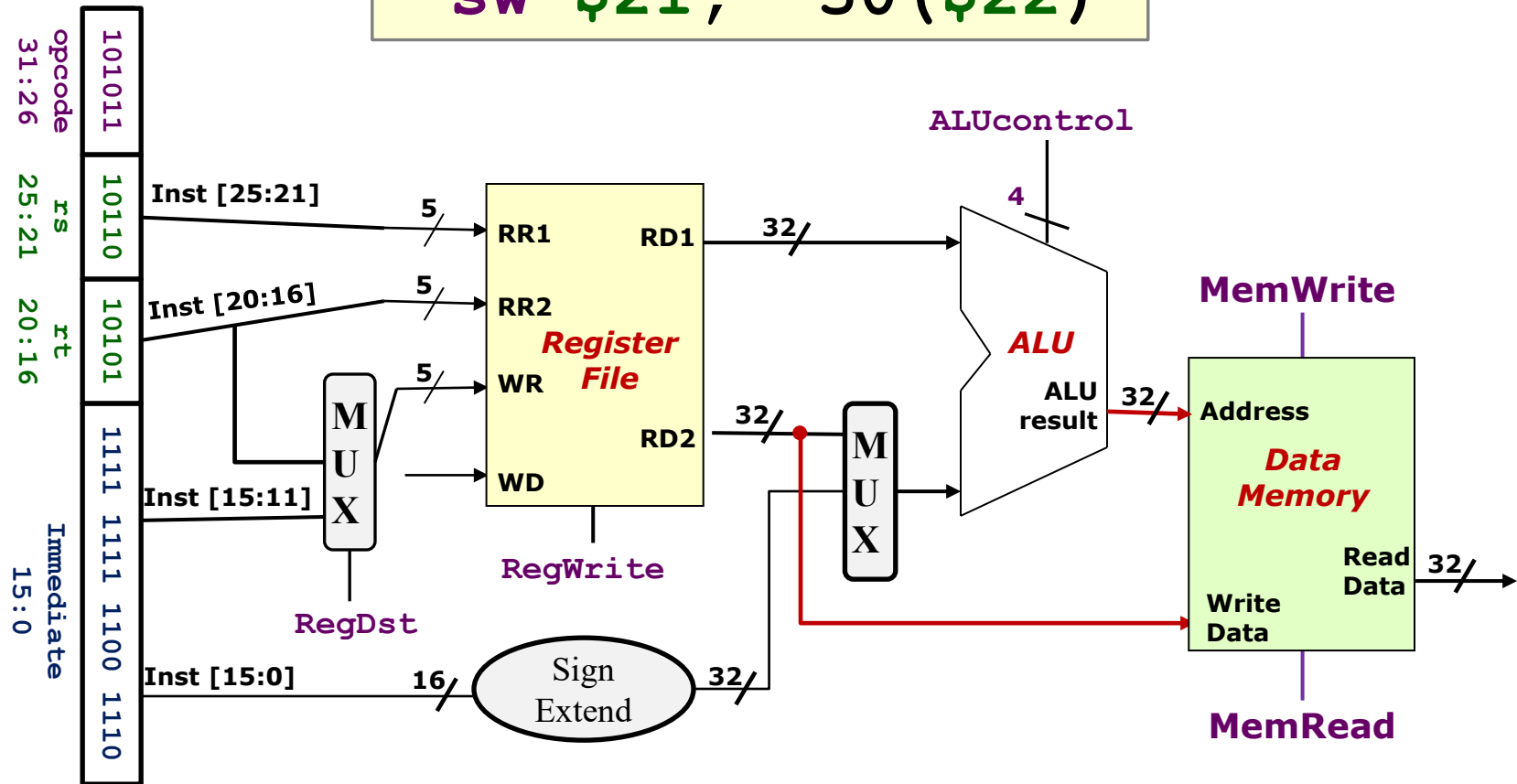

5.4 Memory Stage: Non-Memory Inst.

- Add a multiplexer to choose the result to be stored

add \$8, \$9, \$10

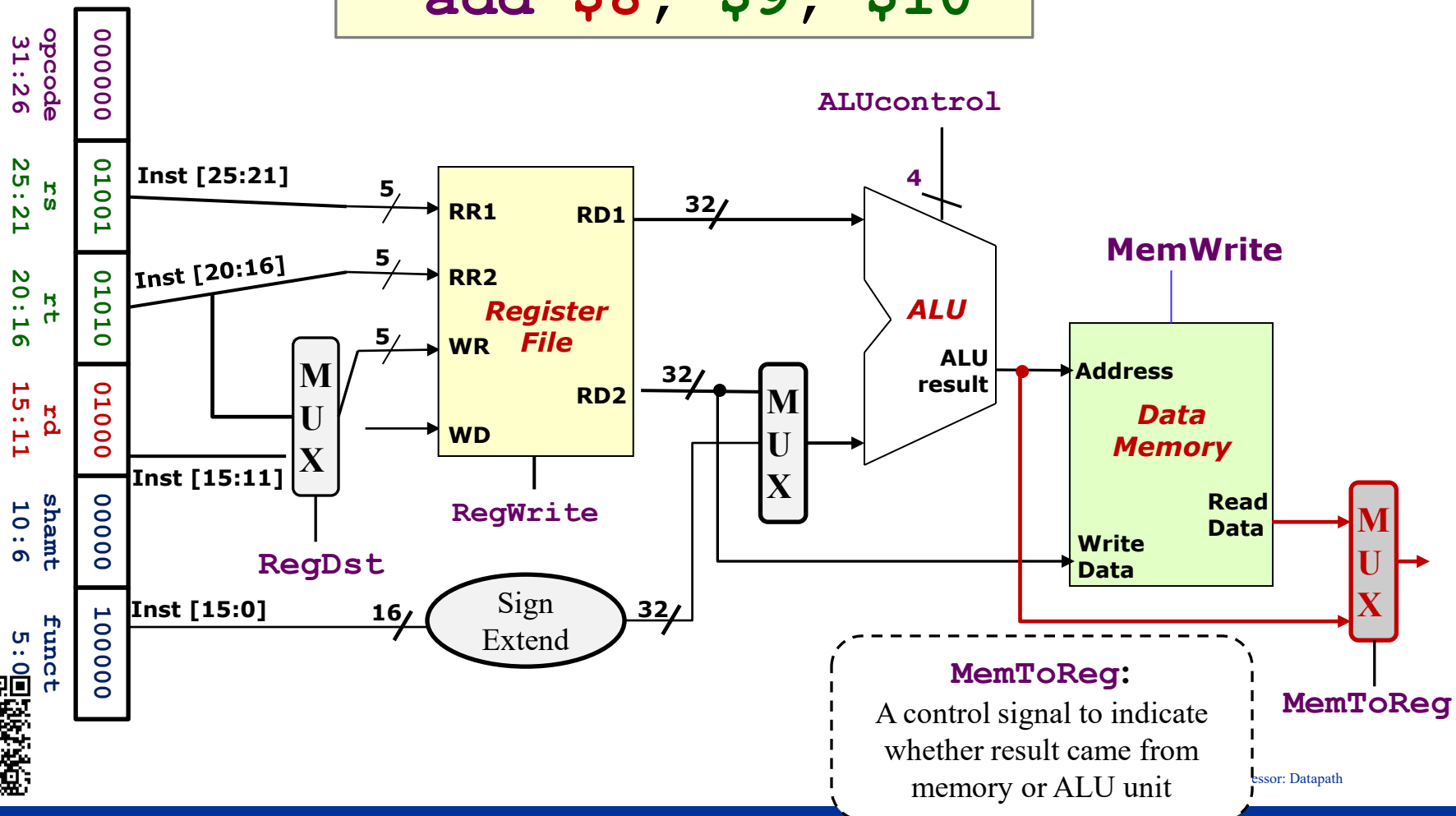

5.5 Register Write Stage: Requirements

1. Fetch
2. Decode
3. ALU
4. Memory
- 5. RegWrite**

■ Instruction Register Write Stage:


- Most instructions write the result of some computation into a register
 - **Examples: arithmetic, logical, shifts, loads, set-less-than**
 - **Need destination register number and computation result**
- Exceptions are stores, branches, jumps:
 - **There are no results to be written**
 - **These instructions remain idle in this stage**

■ Input from previous stage (Memory):

- Computation result either from memory or ALU



5.5 Register Write Stage: Block Diagram

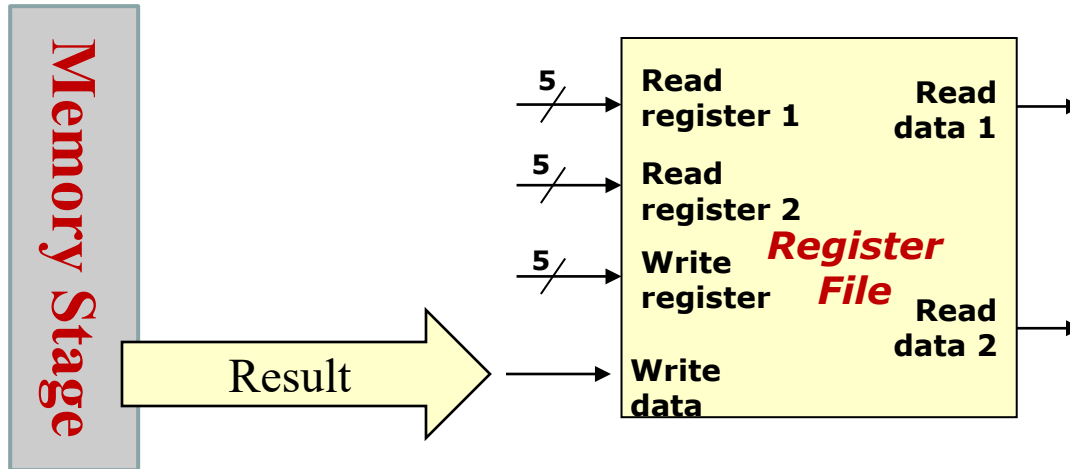


- **Result Write stage has no additional element:**
 - Basically just route the correct result into register file
 - The *Write Register* number is generated way back in the **Decode Stage**



5.5 Register Write Stage: Routing

add \$8, \$9, \$10

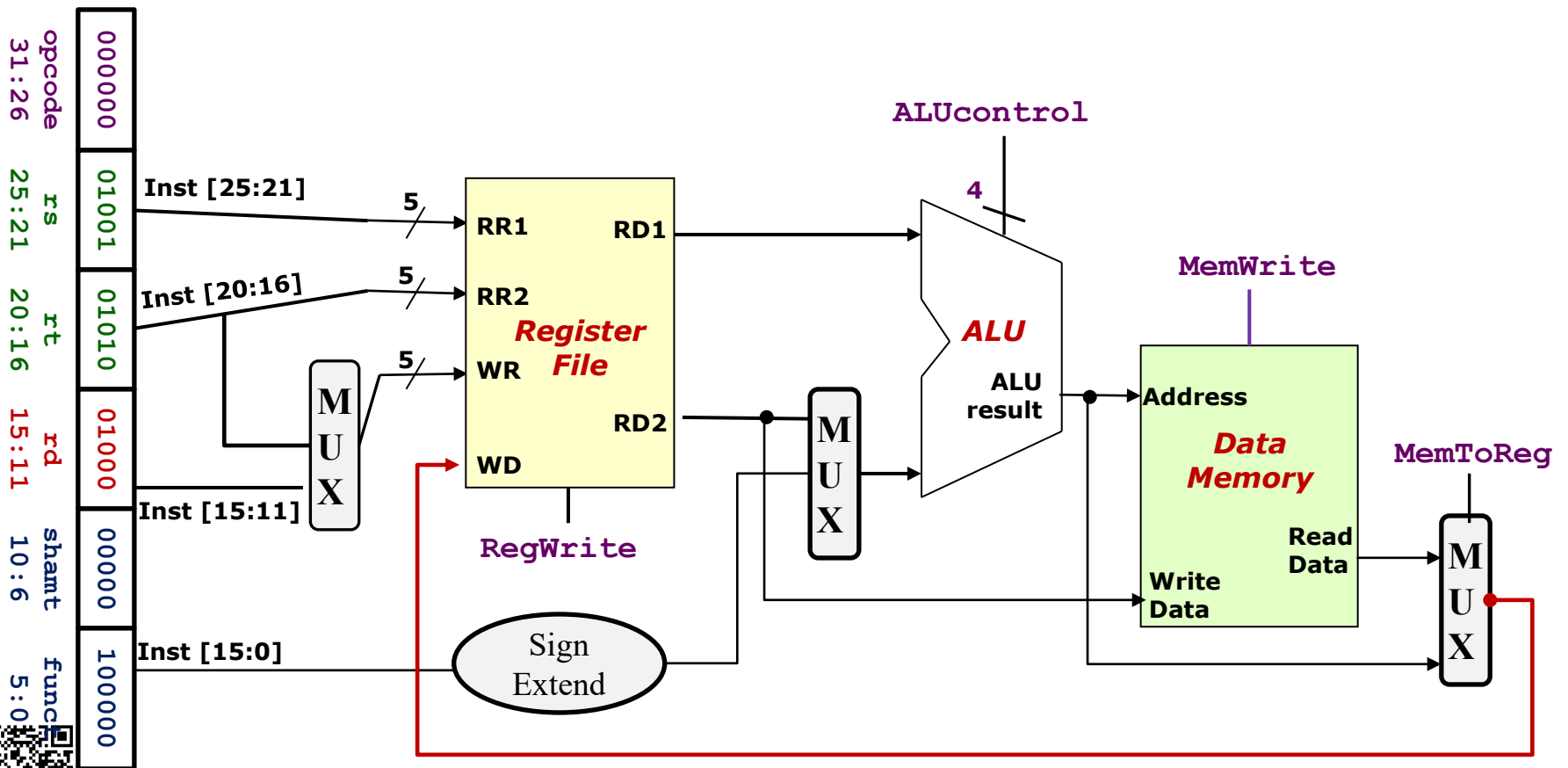

6. The Complete Datapath!

- **We have just finished “designing” the datapath for a subset of MIPS instructions:**
 - Shifting and Jump are not supported
- **Check your understanding:**
 - Take the complete datapath and play the role of controller:
 - **See how supported instructions are executed**
 - **Figure out the correct control signals for the datapath elements**
- **Coming up next: Control**



